

INTEGRATED CIRCUITS

Michael D'Argenio – mjdargen@ncsu.edu
Electrical Engineering – SS 2019 – Duke TIP



Intro to Integrated Circuits (ICs)

- A set of electronic circuits on one small flat piece (or "chip") of semiconductor material.
- Instead of having many discrete components, an IC provides the same functionality in a single package.
- Contain many transistors and other passive components.

ICs

- Some of the ICs we will discuss are:
 - Op-Amps
 - Flip-Flops
 - Comparators
 - 555 Timers
 - Digital Logic Gates
- Many ICs use either TTL or CMOS technology.

CMOS vs. TTL

CMOS vs. TTL Logic

- CMOS – Complementary Metal-Oxide Semiconductor
 - MOSFETs
 - CMOS – uses complementary pairs of n&p MOS
 - Fewer parts, lower power consumption
- TTL – Transistor-Transistor Logic
 - BJTs
 - Stronger against ESD
- Made to implement logic, stay tuned for next week!!

OP-AMPS

Intro to Op-Amps

- Operational amplifiers – a DC-coupled, high-gain electronic voltage amplifier with a differential input and, usually, a single-ended output.
- An op-amp produces an output voltage that is typically hundreds of thousands of times larger than the potential difference between its input terminals.


V_+ : non-inverting input

V_- : inverting input

V_{out} : output

V_{S+} : positive power supply


V_{S-} : negative power supply

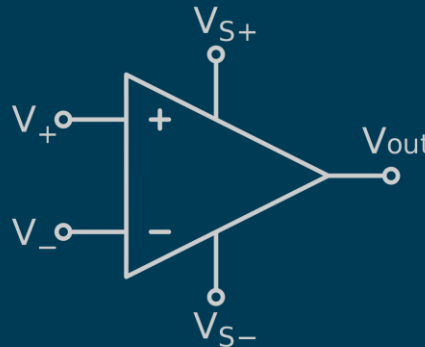


Op Amp Characteristics

- In a closed loop, the output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
- The inputs draw no current.
- Voltage Gain, $A = \frac{V_{out}}{V_{in}}$: $V_{in} = V_+ - V_-$


741 Op Amp

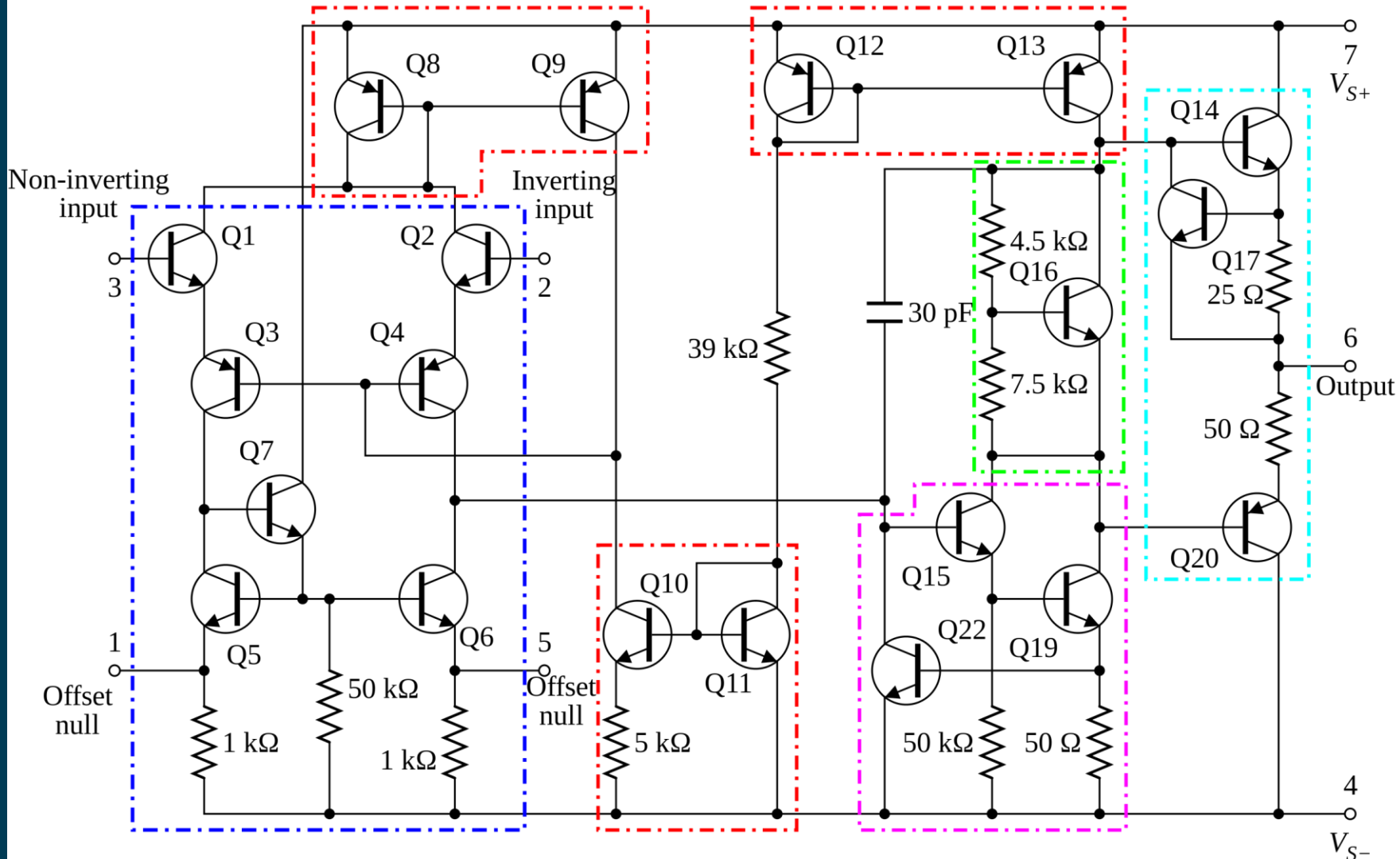


Non-inverting Amplifier

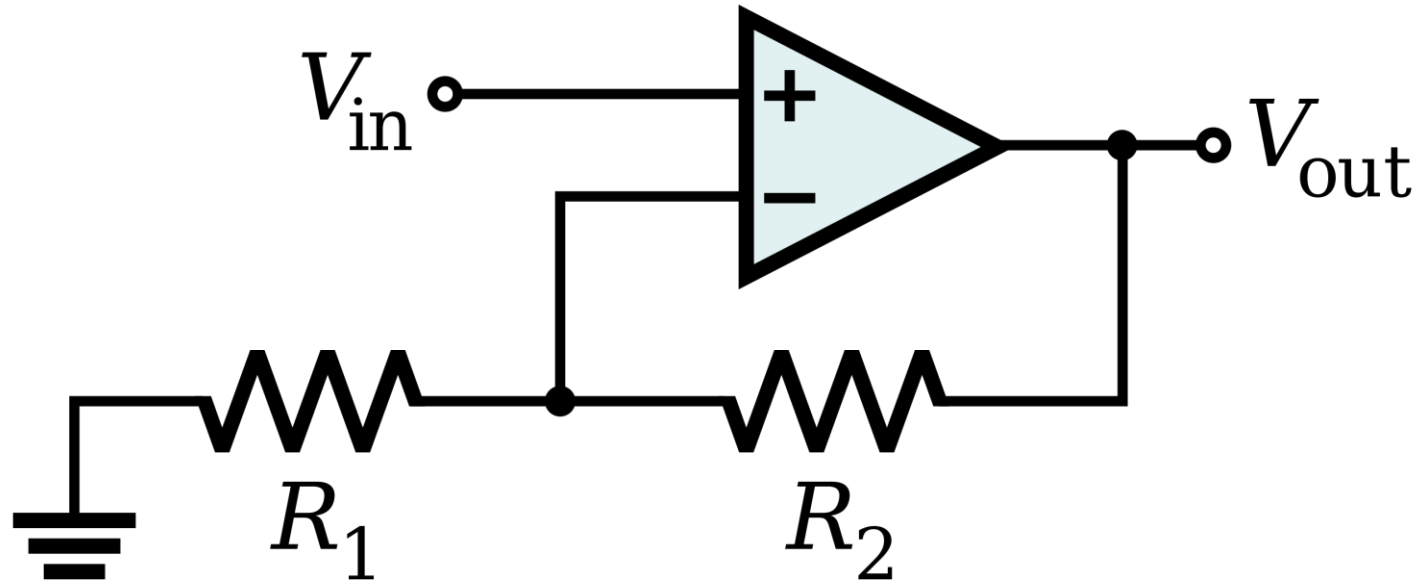

Inverting Amplifier

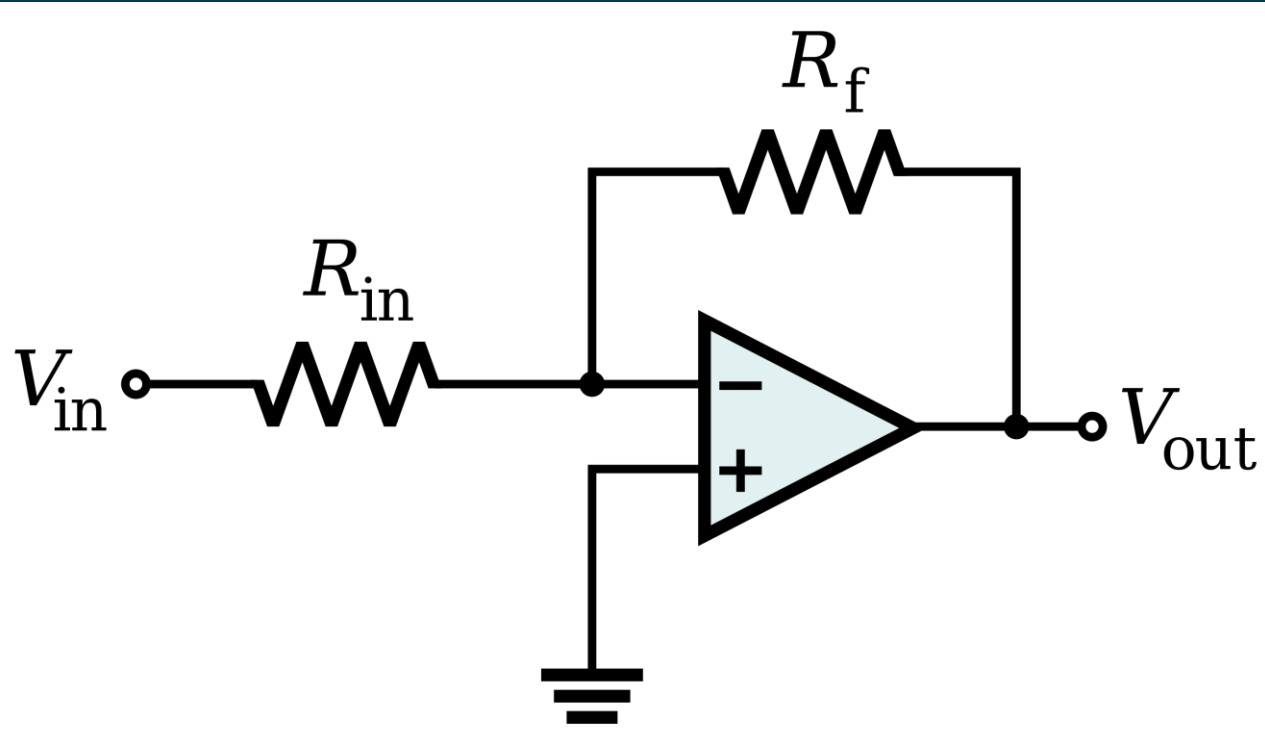


Differential Amplifier

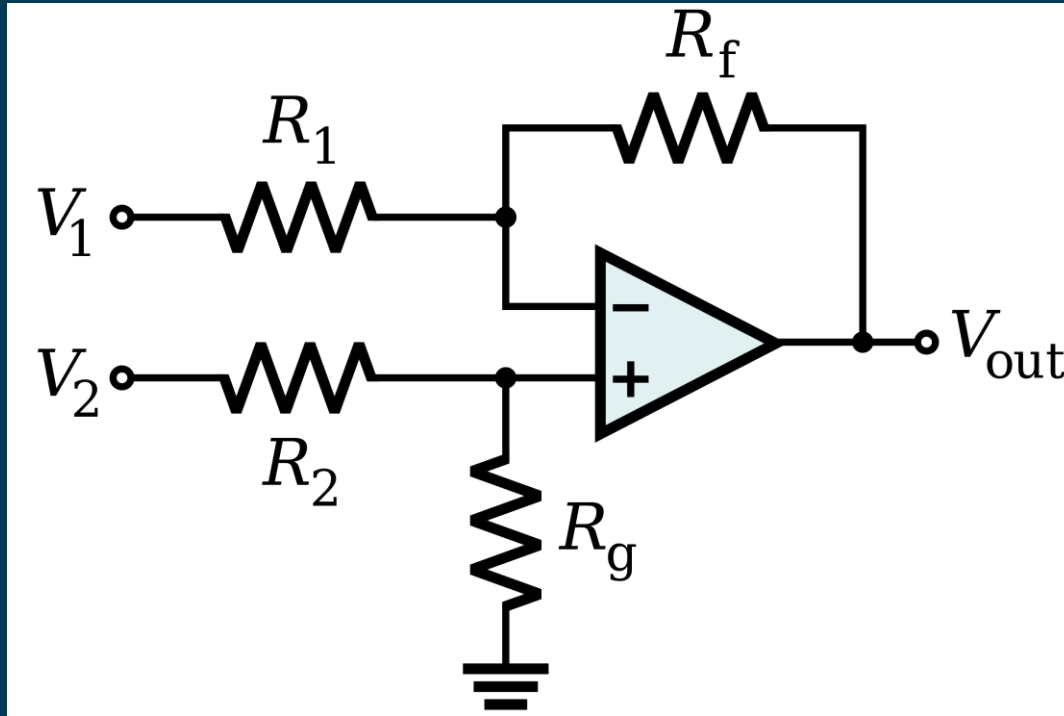

Voltage Follower (Unity Buffer)

- $V_{out} = V_{in}$

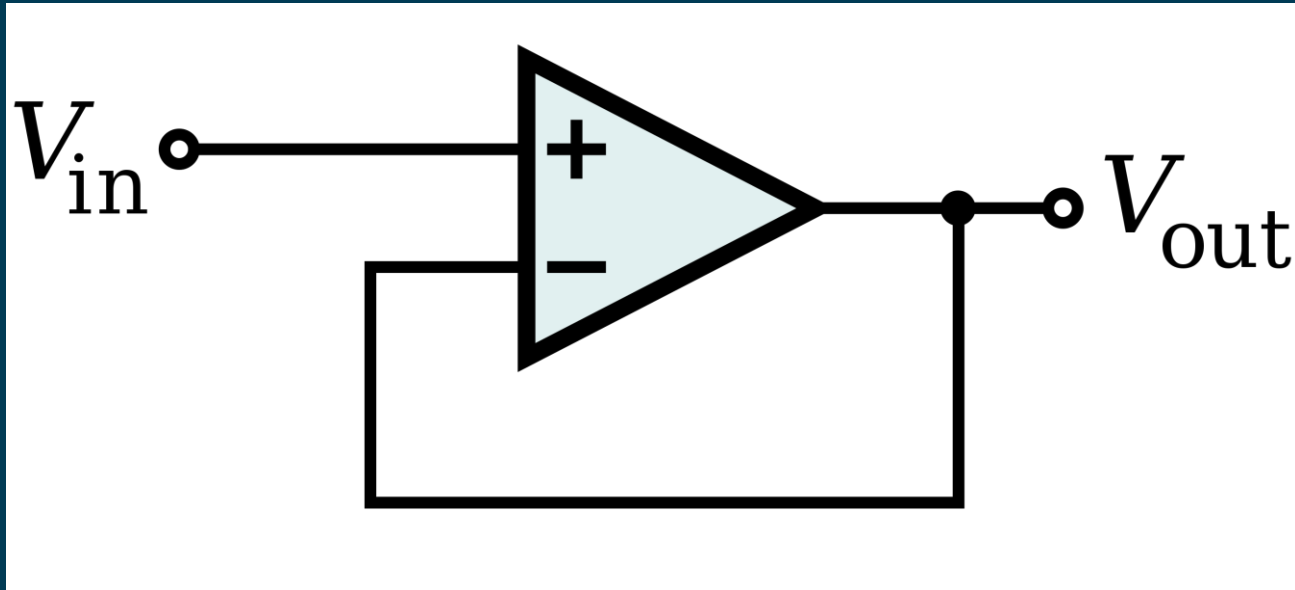


Uses

- Audio video amplifiers and buffers
- Analog math using differentiators and integrators
- Rectifiers and regulators
- Analog-to-digital and digital-to-analog converters
- Oscillators and waveform generators
- Voltage clamping and clipping

COMPARATOR

Comparator

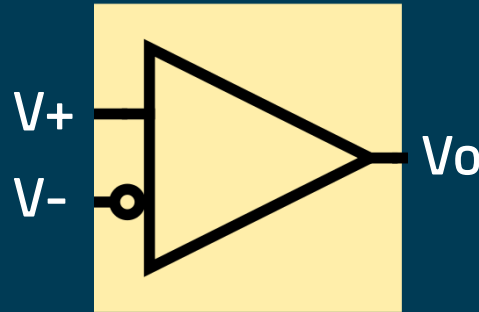- A device that compares two voltages and outputs a digital signal indicating which is larger. It has two analog input terminals V_+ and V_- , and one binary digital output V_o .
- $V_o = 1$; if $V_+ > V_-$
- $V_o = 0$; if $V_+ < V_-$




S-R FLIP FLOP

S-R Flip Flop

- A latch circuit that has two stable states and can be used to store information.
- S – Set, drives output Q high
- R – Reset, drives output Q low
- Q' – an inversion of output Q


S	R	Q
0	0	hold
0	1	0 (reset)
1	0	1 (set)
1	1	Forbidden

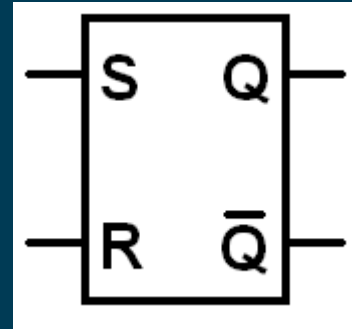


555 TIMER

Intro to the 555 Timer

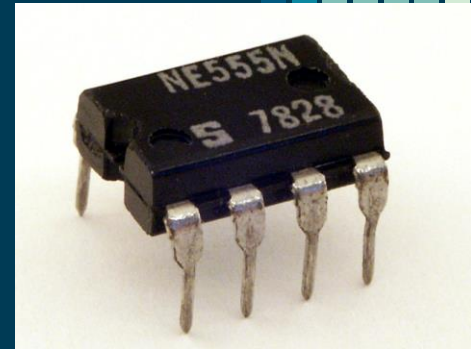- An integrated circuit (chip) used in a variety of timer, pulse generation, and oscillator applications.
- Can be used to provide time delays, as an oscillator, and as a flip-flop element.



555 Timer Block Diagram

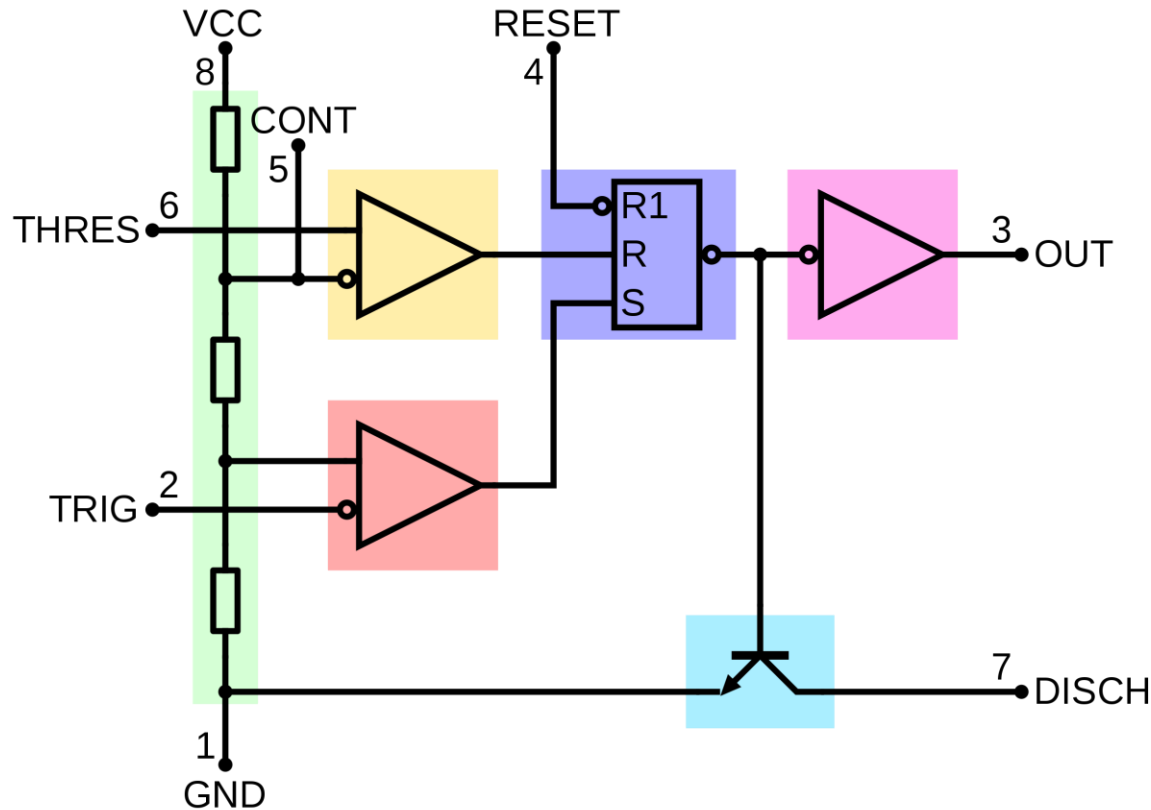

555 Timer Explained

- Green: Between the positive supply voltage V_{CC} and the ground GND is a voltage divider consisting of three identical resistors, which create two reference voltages at $1/3 V_{CC}$ and $2/3 V_{CC}$. The latter is connected to the "Control Voltage" pin. All three resistors are $5\text{ k}\Omega$.
- Yellow: The comparator negative input is connected to higher-reference voltage divider of $2/3 V_{CC}$ (and "Control" pin), and comparator positive input is connected to the "Threshold" pin.
- Red: The comparator positive input is connected to the lower-reference voltage divider of $1/3 V_{CC}$, and comparator negative input is connected to the "Trigger" pin.

555 Timer Explained Continued



- Purple: An SR flip-flop stores the state of the timer and is controlled by the two comparators. The "Reset" pin overrides the other two inputs, thus the flip-flop (and therefore the entire timer) can be reset at any time.
- Pink: The output of the flip-flop is followed by an output stage with push-pull (P.P.) output drivers that can load the "Output" pin with up to 200 mA (varies by device).
- Cyan: Also, the output of the flip-flop turns on a transistor that connects the "Discharge" pin to ground.

555 Timer Operating Modes

- We will focus on two of the possible 555 timer modes.
- Astable (free-running) mode – the 555 can operate as an electronic oscillator. Uses include LED and lamp flashers, pulse generation, logic clocks, tone generation, security alarms, pulse position modulation and so on.
- Monostable mode – in this mode, the 555 functions as a "one-shot" pulse generator. Applications include timers, missing pulse detection, bounce-free switches, touch switches, frequency divider, capacitance measurement, pulse-width modulation (PWM) and so on.



Astable Mode (free-running)

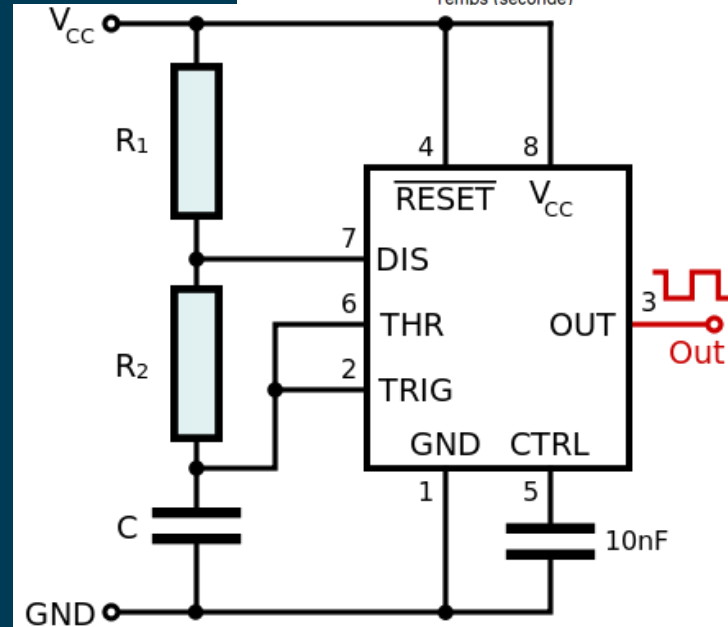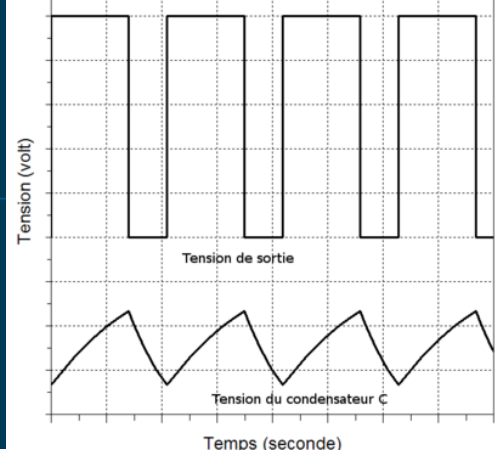- Puts out a continuous stream of rectangular pulses having a specific frequency determined by R_1 , R_2 , C .
- Output high when trigger less than $1/3 V_{cc}$, low when threshold greater than $2/3 V_{cc}$.
- $$f = \frac{1}{0.693 \times C \times (R_1 + 2R_2)}$$
- $$t_{high} = 0.693 \times C (R_1 + R_2)$$
- $$t_{low} = 0.693 \times C \times R_2$$



Monostable

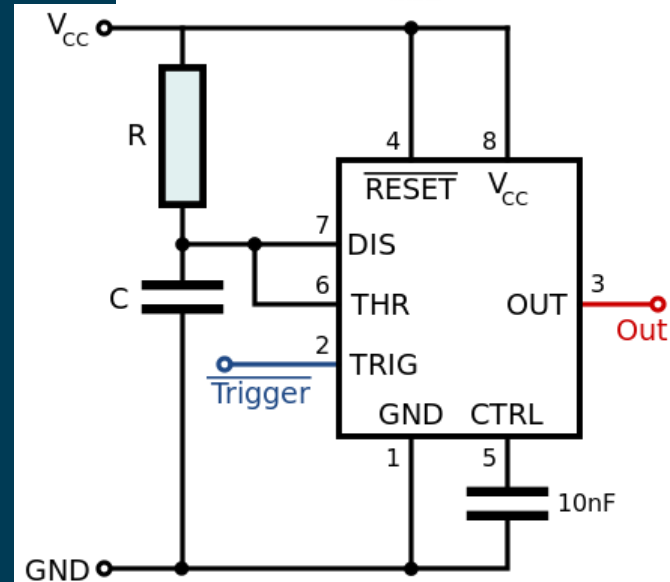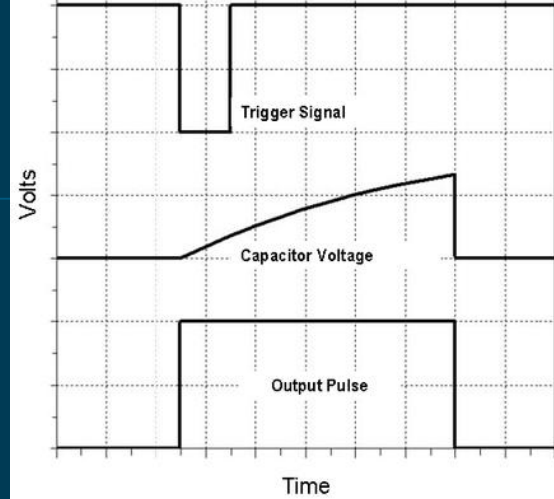- Similar to astable but requires external trigger (driven by another source).
- Output driven high when trigger drops below $1/3 V_{CC}$, and driven low when the threshold charges to $2/3 V_{CC}$.
- $t_{pulse} = 1.099 \times RC$



LOGIC ICs

Logic ICs

- Uses multiple transistor to implement digital logic.
- What's digital?
- More next week!



